



From above diagram,

$$s^* = (S \cdot \text{clk})' = S' + \text{clk}'$$

$$R^* = (R \cdot \text{clk})' = R' + \text{clk}'$$

let us evaluate circuit 1 without clock

S^*	R^*	Q	\bar{Q}
0	0	Not used	
0	1	1	0
1	0	0	1
1	1	Memory of previous state	

Table 1

Now, let us evaluate s^* & R^* when clock turns 0 & 1 without not gate in the beginning.

when clock = 1

$$s^* = S'$$

$$R^* = R'$$

when clock = 0

$$s^* = 1$$

$$R^* = 1$$

since in NAND gate, when any input is 0, output is 1 always

let us check Q & \bar{Q} with S & R with clock

clock	S	R	Q	\bar{Q}	from table ①
0	*	*			Memory of previous
$S^* = 1 \Rightarrow 1$ $R^* = 1$	0	0			Memory of previous
$S^* = 1 \leftarrow 1$ $R^* = 0$	0	1	0	1	
1	1	0	1	0	
1	1	1			Not used

Characteristic table

clock	S	R	$Q(1)$
0	*	*	$Q(0)$
1	0	0	$Q(0)$
1	0	1	0
1	1	0	1
1	1	1	Not used

Now, when NOT gate is put in between S & R & single input is given;
Truth table

clk	A	$Q(1)$
0	*	$Q(0)$
1	0	0
1	1	1

(Q-2) Write an assembly language program to multiply two numbers:

soln:-

	Oper ⁿ
D	+ 0 0 C
E	if B 1 F
F	* C A C
G	- B 1 B
H	goto E
I	END

∴ final output is stored in C.

(Q-3) Write an assembly language program to divide two numbers.

→ soln:-

	Operation
F	+ 0 0 C
G	- A B A
H	+ C 1 C
I	comp A 1 D
J	if D G K
K	comp A -1 E
L	if E N M
M	- C 1
N	END

∴ final quotient is stored in C.